


Module 3

Processor Organization & Architecture

Prepared by:
Prof. Datta Deshmukh

Half adder: Definition and Block diagram

 - Performs the addition of two single bit numbers (A and B) and generates two outputs (Sum and Carry)
- From left side, the inputs 'A' & 'B' are applied, while to the right side, the outputs 'SUM' and 'CARRY' are obtained as shown below:



Half adder: Truth table, Equations and Logical diagram

- For two inputs 'A' & 'B', the 'Sum' & 'Carry' outputs are shown below in the Truth table:


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

The output equations are:

$$\text{SUM} = A \sim . B + A . B \sim = (A) \text{ EXOR } (B)$$


$$\text{CARRY} = A . B$$

Logical diagram of Half adder is:

 

Full adder: Definition and Block diagram

 - Performs the addition of three single bit numbers (A , B and C_{in}) and generates two outputs (Sum and Carry Output)
- From left side, the regular inputs ' A ' & ' B ' alongwith input carry ' C_{in} ' are applied, while to the right side, the outputs sum (S) and carry output (C_{out}) are obtained as shown below:



Full adder: Truth table & Output equations

INPUTS			OUTPUTS	
A	B	C _{in}	SUM	CARRY _{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}\text{Sum} &= \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in} \\ &= (A) \text{ EXOR } (B) \text{ EXOR } (C_{in})\end{aligned}$$


$$\begin{aligned}\text{Carry} &= \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in} \\ &= A B + A C_{in} + B C_{in}\end{aligned}$$

Full adder: Equations and Logical diagram


$$\begin{aligned} \text{Sum} &= \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in} \\ &= (A) \text{ EXOR } (B) \text{ EXOR } (C_{in}) \end{aligned}$$

$$\text{Carry} = \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in}$$

$$= A B + A C_{in} + B C_{in}$$

 

 Full adder design by cascading two half adders



- First Half Adder (left side) performs addition of two single bit numbers: 'A' & 'B'
- Second Half Adder (middle) performs the addition of sum bit of the first half adder with the carry input 'C'
- Second Half Adder generates the final 'Sum' output of the Full adder
- The carries generated by both the adders are merged together by 'OR' gate to generate the final output 'Carry'
- The block diagrams can be replaced by the logical diagrams of the half adders


Multiplexer: The general concepts

- Multiplex means 'Many to one'
- Hence, Multiplexer (MUX) has many inputs and one output line
- MUX has 'n' select lines, used to select one out of ' 2^n ' inputs and the logic on the selected input line is steered on the single output line

Common MUXs include:


1. 4:1 MUX (4 inputs, 1 output and 2 select lines)
2. 8:1 MUX (8 inputs, 1 output and 3 select lines)
3. 16:1 MUX (16 inputs, 1 output and 4 select lines)

 4:1 MUX : Block diagram, Truth table & Logical diagram



Truth table of 4:1 MUX

Select lines		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

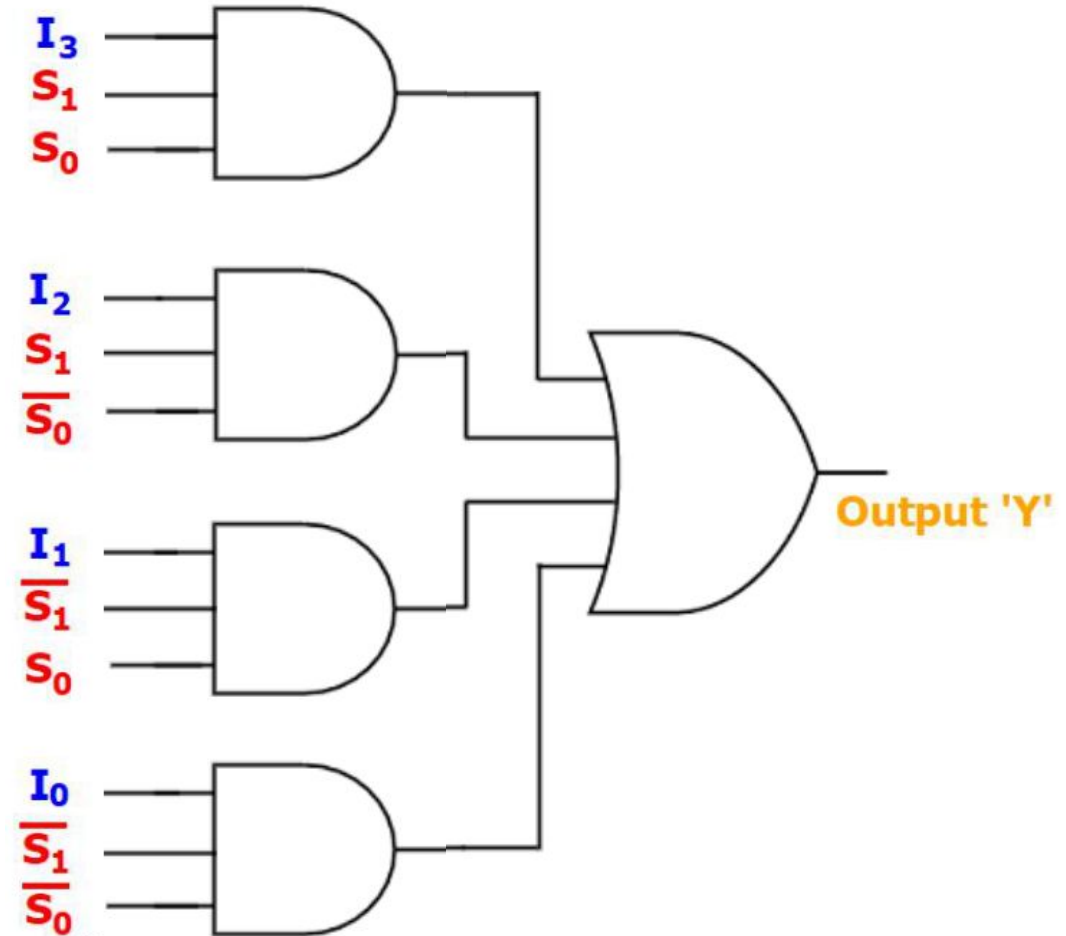


Demultiplexer: The general concepts

- Demultiplex means 'One to Many'
- Hence, Demultiplexer (DEMUX) has one input and many output lines
- DEMUX also has 'n' select lines, used to select one out of '2ⁿ' output lines and the logic on single input is steered to the selected output line

Common DEMUXs include:


1. 1:4 DEMUX (1 input, 4 outputs and 2 select lines)
2. 1:8 DEMUX (1 input, 8 outputs and 3 select lines)
3. 1:16 DEMUX (1 input, 16 outputs and 4 select lines)

 1:4 DEMUX : Block diagram, Truth table & Logical diagram



Select lines		Outputs			
S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

Data input ' I '

 

Encoders: Theory and types

- Encodes the inputs into the output coded data
- When any one of the input is activated, the output code is generated


Octal to Binary encoder (8:3 encoder)

When one of the input (out of 8 inputs) is activated, then 3 bit binary sequence number of the activated input is generated

Decimal to BCD encoder (10:4 encoder)

When one of the input pertaining to decimal values '0' to '9' is activated, then the output is 4 bit BCD equivalent of that activated input

 8:3 (Octal to Binary) encoder: Block diagram to Design




Truth Table										
Inputs								Outputs		
MSB							LSB			
I ₇	I ₆	I ₅	I ₄	I ₃	I ₂	I ₁	I ₀	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Output Equations:


$$Y_0 = I_1 + I_3 + I_5 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

 

 Decimal to BCD encoder: Block, Truth table, Equations



Output Equations:

$$Y_0 = I_1 + I_3 + I_5 + I_7 + I_9$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

$$Y_3 = I_8 + I_9$$

Truth Table

Inputs										Outputs			
MSB I_9	I_8	I_7	I_6	I_5	I_4	I_3	I_2	I_1	LSB I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1


Decoder: Theory and types

- Accepts the coded information as the input and activates one particular output line
- Normally, the input coded information is in Binary

Decoders are of the following types:


1. 2:4 Decoder (2 inputs and $2^2 = 4$ outputs)
2. 3:8 Decoder (3 inputs and $2^3 = 8$ outputs)
3. 4:16 Decoder (4 inputs and $2^4 = 16$ outputs)
4. BCD to Seven Segment Decoder (4 bit BCD input & 7 segment outputs)

 2:4 and 3:8 Binary Decoders with active high outout (Block diagram & Truth table)




Truth Table

A	B	Q ₀	Q ₁	Q ₂	Q ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

a	b	c	y ₀	y ₁	y ₂	y ₃	y ₄	y ₅	y ₆	y ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 Practical 3:8 Decoder with active low output (IC 74 LS 138)




Inputs						Output							
Enable			Select										
G2A	G2B	G1	C	B	A	0	1	2	3	4	5	6	7
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0


Clocked SR flip-flop: Design, Symbol, Truth table & Operation

Designed using SR latch (NAND gate #3, #4) and Steering logic (NAND #1, #2)

Logical design & symbol:

 

Holds 1 bit info.

 

Truth table (with CLK present, CLK = 1)

S	R	Q	State
0	0	Previous State	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Forbidden

When S = R = 0: #1 = #2 = 1. Hence, #3 & #4 maintains previous state

When S = 0, R = 1: #1 = 1, #2 = 0. It makes, $Q\sim = 1$. Hence, $Q = 0$. Output is Reset.

When S = 1, R = 0: #1 = 0, #2 = 1. It makes, $Q = 1$. Means, Output is Set.

When S = R = 1: Makes #1 = #2 = 0. Hence, #3 = #4 = 1 simultaneously (impossible)

When CLK = 0:


O/Ps of NAND#1 & #2 = 1. The latch (NAND#3, #4) maintains **previous state**

When CLK = 1:

Depending upon S & R inputs, **proper output obtained as per the truth table**

JK flip-flop: Design, Symbol, Operation & Truth table

 Using SR flipflop & feedback Operation of JK flip-flop:




When $J = K = 0$: Makes $S = R = 0$. Hence, previous state is maintained.

When $J = 0, K = 1$: Makes $S = 0$ & hence, $Q = 0$

When $J = 1, K = 0$: Makes $R = 0, Q^{\sim} = 0$. Hence, $Q = 1$

 
When $J = K = 1$: Output toggles (changes state)



Truth table of JK flip-flop:


J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	\overline{Q}_0 (toggles)

Symbol of

 

Toggle (T), Delay (D) using JK flip flop: Design, Truth table

T flip flop using JK flip flop & symbol

 


Truth table of T flip flop

Input T	Outputs	
	Present State Q_n	Next State Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

When T = 0, maintains previous state
T flip flops are used in counter designs

D flip flop using JK flip flop & symbol

 

Truth table of D flip flop

Input D	Outputs	
D	Q_n	Q_{n+1}
	0	0
0	1	0
1	0	1
1	1	1

D	Q	\bar{Q}
0	0	1
1	1	0

Delay flip flop transfers the logic of D input to the output after 1 CK pulse (generates a delay of 1 CK)

Used in the design of digital delay lines

CPU (Processor) Register Organization

- 2 major types of registers:
 - User visible registers
 - Control & status registers
- User visible registers:
 - These are General Purpose Registers (GPRs) which hold data at the time of processing.
 - Some of the registers are also used to address memory.
- Control & status registers:
 - Used to control the operation of the processor.
 - Most of these registers are not visible to the user

User visible (available) registers of the Processor

- User visible address registers include segment registers, Index registers, Stack Pointer
- Segment register:
 - Holds the base address of the segment.
 - Multiple segment registers such as data segment register, code segment register, stack segment register etc.
- Index registers: Used for indexed addressing
- Stack pointer: Points the “Top of the stack” in execution of
 - PUSH, POP instructions
 - Procedure calls
 - Interrupt processing

Control & Status registers of the Processor

- Condition codes or flags: Individual bits that are set/reset by the CPU as result of operation
- Program counter (PC): Points the address of the next instruction to be fetched
- Instruction Register (IR): Contains the Op-code of the instruction to be executed
- Memory address register (MAR): Points memory address while fetching data/operand
- Memory buffer Register (MBR): Holds the data to be read from or written into the memory

Instruction format

- Instruction format depends upon type of the instruction

Addressing modes of the generic Processor

Defines the method to refer data/operand

Common addressing modes:

- 1) Immediate addressing mode
- 2) Direct addressing mode
- 3) Indirect addressing mode
- 4) Register addressing mode
- 5) Register Indirect addressing mode
- 6) Displacement addressing mode
- 7) Stack addressing

Immediate Addressing mode


Instruction



- Data defined as immediate number within instruction
- Example: Intel 8085 instruction, ADI 20
Adds data (20)H to accumulator


Direct Addressing mode

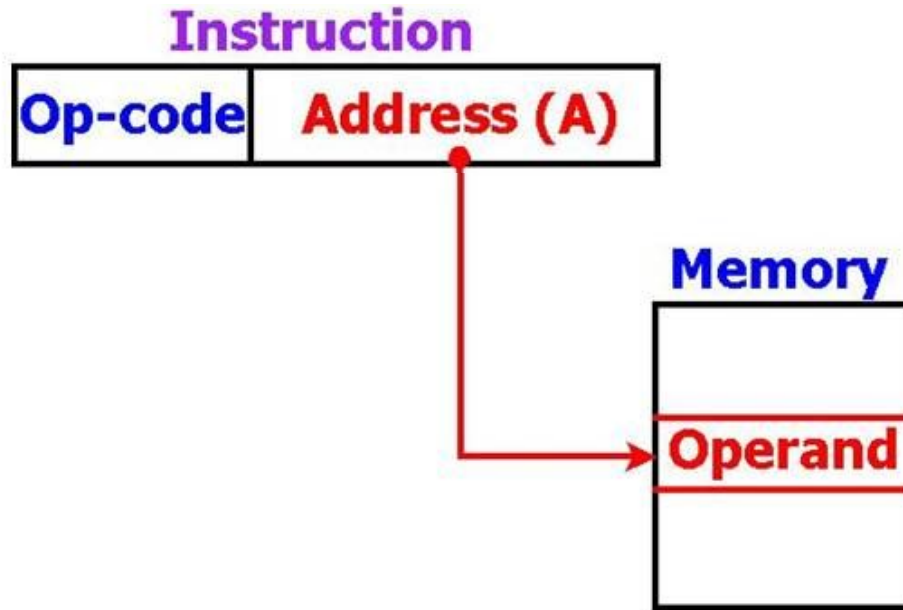- Address of operand (data) is defined directly within instruction



- Example: Intel 8085 instruction : LDA 1000
Loads 8 bit data from address (1000)H to accumulator

Indirect Addressing mode

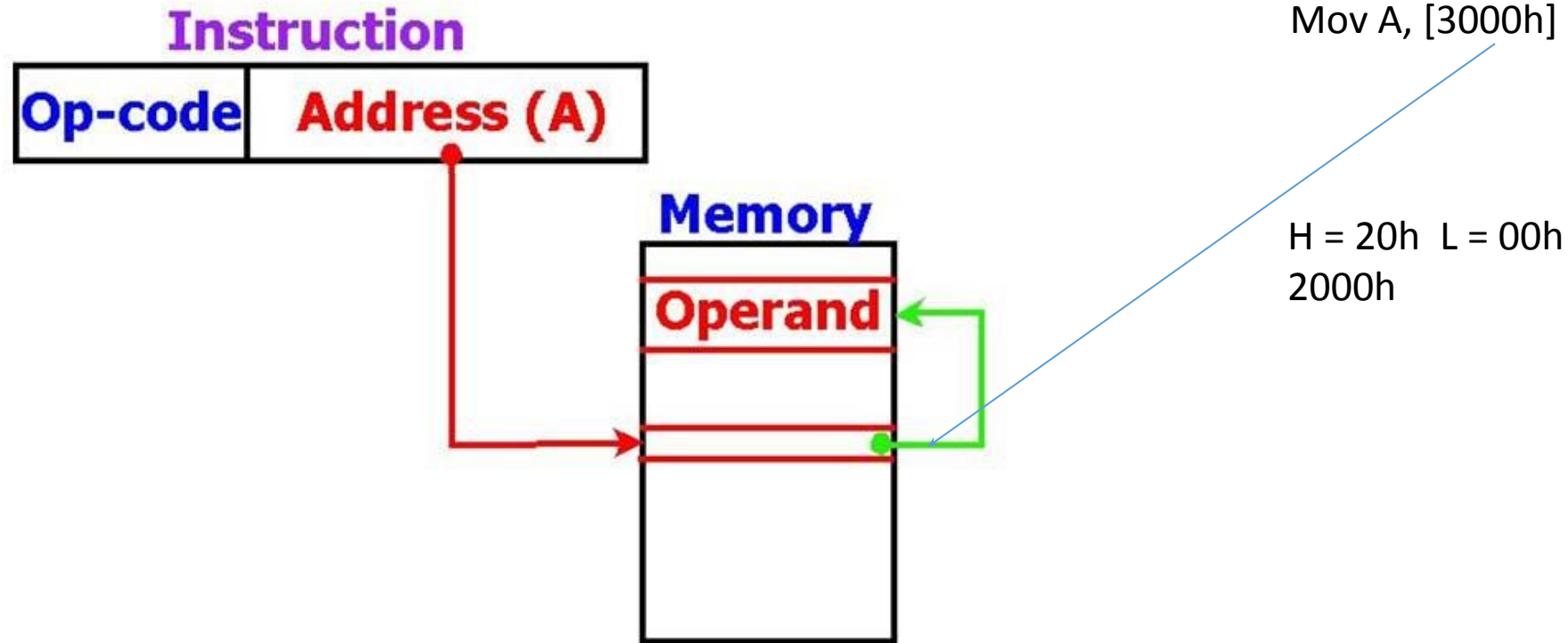


Bracket indicates indirect addressing

- Address “A” points memory location
- This memory location points another memory location that has the operand

Register Addressing mode

- Operand is defined in register
- Register-ID is defined within the instruction


MOV A, L

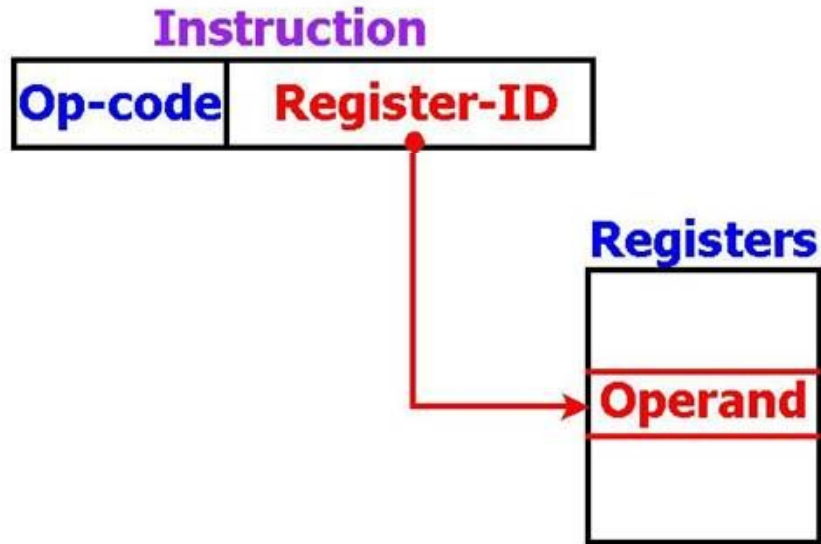

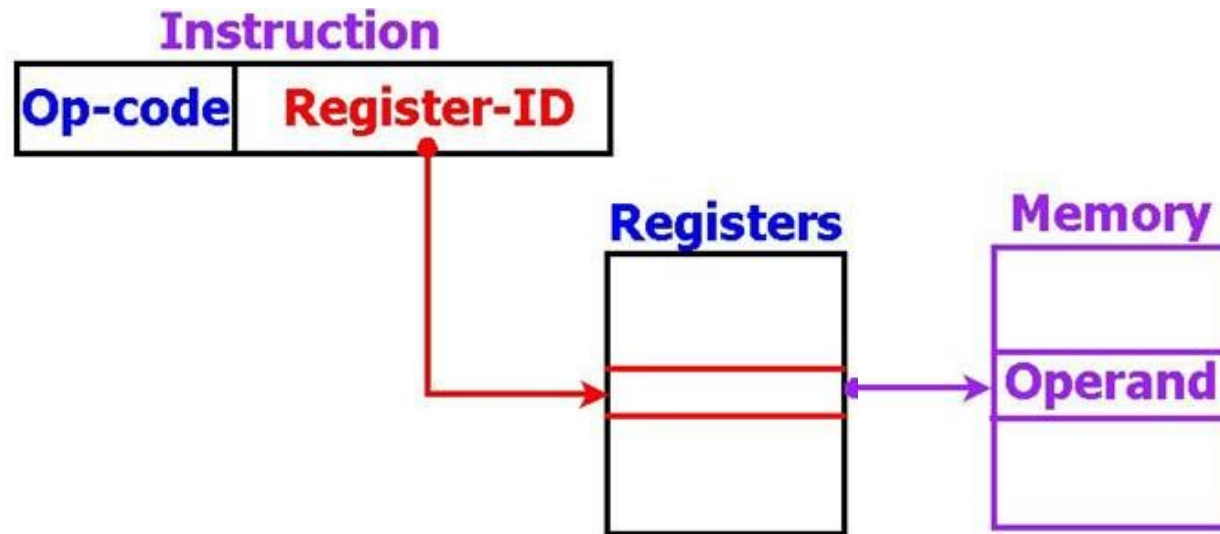- Example: Intel 8085 instruction, ADD B
Adds register B contents to accumulator

Register Indirect Addressing mode


- Register or register pair defines the address of the operand



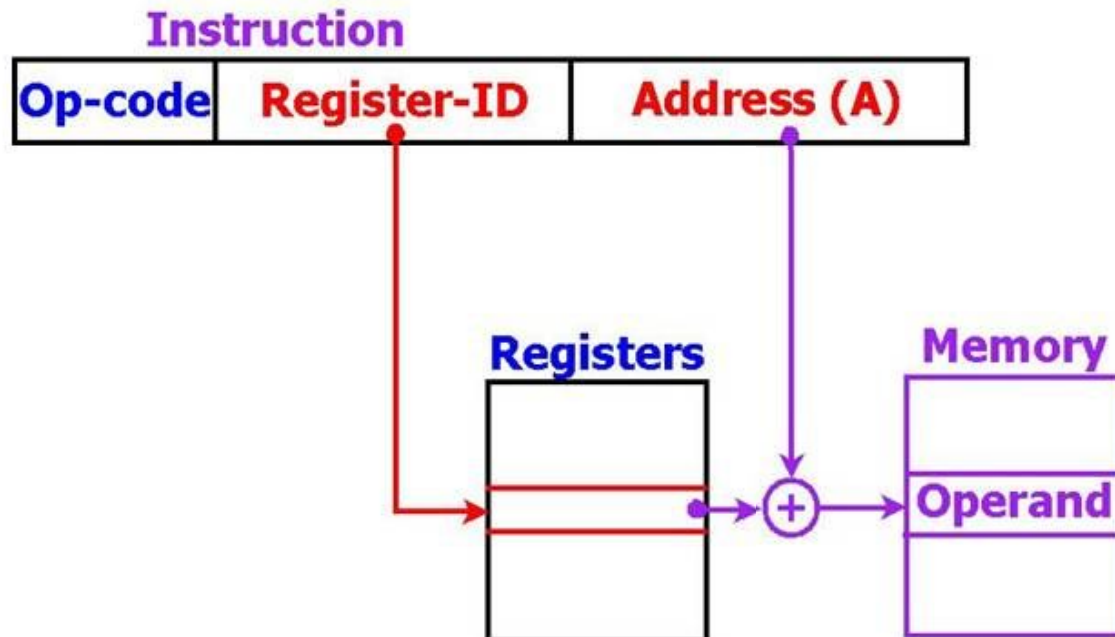- Example: Intel 8085 instruction, ADD M
Adds contents of memory location
(pointed by HL register pair) to accumulator

Displacement Addressing mode

- Address of the operand = Contents of register + Offset address (A)
- Both Register-ID & Offset address (A) are defined within the instruction



Stack Addressing mode

- Data stored on stack memory
- Stack memory is pointed by stack pointer
- Data accessed by using 2 instructions:
 - PUSH: Data copied onto stack
 - POP: Data retrieved out of stack

Instruction formats of Intel 8085 Processor

Single Byte format

- It contains only one byte i. e. Op-code byte.
- Op-code may specify operation alongwith the register-ID
- Register addressing mode or indirect addressing uses single byte format in 8085 Processor

Two Byte format

- It contains two bytes: First byte is op-code & second byte contains immediate 8 bit data or I/O port address
- Immediate addressing mode uses this format

Three Byte format


- It contains three bytes: First byte is op-code, Second byte is lower byte of 16 bit data or address & third byte is upper byte of 16 bit data or address
- Direct addressing or Immediate addressing (for 16 bit data) uses this format

Instruction cycle of the Processor

It is the time required to execute one complete instruction

- Instruction Cycle = **Fetch cycle + Execute cycle**
- **Fetch:** Reading instruction from memory
- **Execute:** Performing the operation

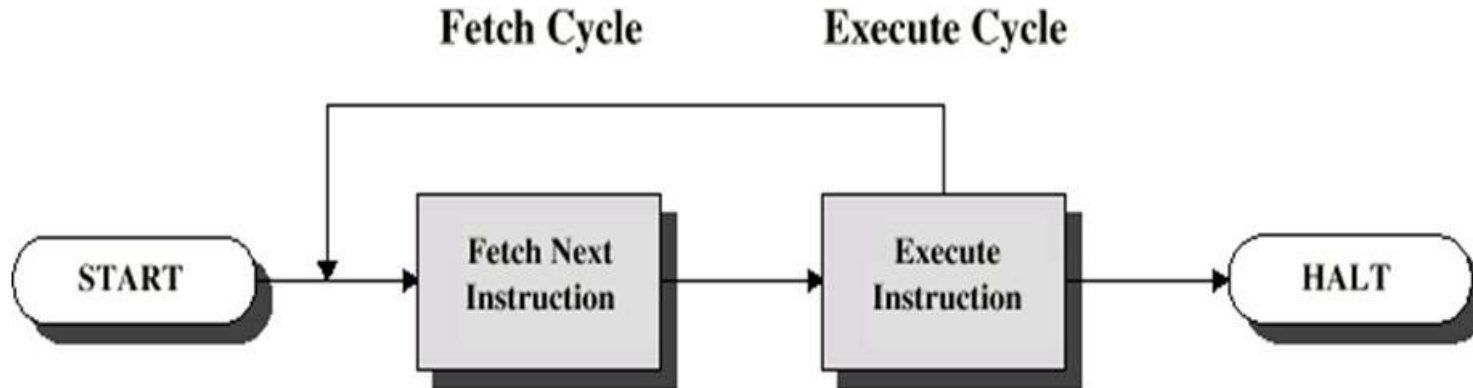$I\ C = \text{fetch} + \text{decode} + \text{execute}$



Fetch Cycle

- **Program Counter (PC) holds the address of next instruction to be fetched**
- **Processor fetches instruction op-code from memory address pointed by PC**
- **Instruction op-code gets loaded into Instruction Register (IR)**
- **PC is automatically incremented to point the address of the next instruction**

Execute Cycle

- Processor decodes/interprets instruction
- Decoding of the instruction is done by using internal instruction decoder
- Decoded instruction is then executed inside ALU (ALU performs the intended operation)
- Execution includes data processing operation (either arithmetic or logical operation on data)
- For every instruction, such fetch & execute cycles are repeated

Instruction Interpretation and Sequencing

Instruction Interpretation:

- Instructions are stored in the memory in the form an Op-code (Operation Code)
- Op-code is unique hexadecimal code for each assembly language instruction
- Op-code must be decoded by the Processor internally using Instruction Decoder
- Instruction decoding decides the action to be performed by the Processor
- Hence, Instruction Decoding = Instruction Interpretation
- After decoding the instruction, the internal control unit generates the control signals for execution of the instruction in the ALU section

Instruction sequencing:

- Performed by loading proper address in the Program Counter (PC) or similar register of the Processor
- Once loaded with address, the PC always points address of the next instruction to be executed and is auto-incremented after completion of current instruction